



## Portfolio Assessment tool

<b>Qualification national code and title</b>	<b>UEE30811 - Certificate III in Electrotechnology: Electrician</b>
<b>Unit/s national code/s and title/s</b>	<b>UEENEEG033A – Solve problems in single and three phase low voltage electrical apparatus and circuits - Heating</b>

<b>Portfolio Assessment</b>			
<b>Solve problems in single and three phase low voltage electrical apparatus and circuits G033A Heating</b>			
<b>Lecturer Name</b>			
<b>Student Name</b>			
<b>Student ID Number</b>			
<b>Telephone Contact Number</b>		<b>Email:</b>	
<p>By completing and submitting this signed form to my lecturer, I am stating that:</p> <ul style="list-style-type: none"> <li>a. The attached submission is completely my own work</li> <li>b. I understand a copy of my assessment will be kept by the NMTAFE for their records</li> <li>c. I understand my assessment may be selected for use in the NMTAFE's validation and audit process to ensure student assessment meets requirements</li> </ul>			
<b>Student Signature</b>		<b>Date</b>	
<b>Due Date</b>		<b>Time</b>	

**Assessment Result Satisfactory / Not Yet Satisfactory** (please circle)      **Date:** \_\_\_\_\_

*In order to satisfy requirements for this assessment, you need to complete the following:*

<p><b>Feedback to student:</b></p> <p><b><u>Assessor please note:</u> Where verbal clarification has been sought from a student to gather additional assessment evidence from an assessment item, question/s and response/s must be recorded, signed, and dated by the assessor, against the relevant assessment item/s.</b></p>
--

**Student Feedback**

<p><b>Feedback from student:</b></p>
--------------------------------------

**Lecturer Signature:** \_\_\_\_\_ **Student Signature:** \_\_\_\_\_



## Portfolio Assessment tool

<b>Qualification national code and title</b>	UEE30811 - Certificate III in Electrotechnology: Electrician
<b>Unit/s national code/s and title/s</b>	UEENEEG033A – Solve problems in single and three phase low voltage electrical apparatus and circuits - Heating

### Assessment type (☑):

- Questioning (Oral/Written)
- Practical Demonstration
- 3<sup>rd</sup> Party Report
- Other – Project/Portfolio (*please specify*)

### Assessment Resources:

Students will need access to:

Writing Instruments  
Three Heat Switch panel

### Assessment Instructions:

#### Assessor instructions

1. Student to answer all portfolio question by due date.
2. The assessor is to sign and record the students result as **satisfactory** or **not yet satisfactory** at the end of the assessment.

#### Student instructions

1. *Complete all portfolio questions by the due date given to you by your lecturer.*
2. ***Failure to submit by due date will result in a re-enrol for this unit.***



## Portfolio Assessment tool

<b>Qualification national code and title</b>	<b>UEE30811 - Certificate III in Electrotechnology: Electrician</b>
<b>Unit/s national code/s and title/s</b>	<b>UEENEEG033A – Solve problems in single and three phase low voltage electrical apparatus and circuits - Heating</b>

1. In the spaces provided below, sketch a **full circuit diagram** (including the elements) demonstrating how a “Three-Heat” switch achieves each of its 3 different heat settings.

**Low**

**Medium**

**High**



## Portfolio Assessment tool

<b>Qualification national code and title</b>	<b>UEE30811 - Certificate III in Electrotechnology: Electrician</b>
<b>Unit/s national code/s and title/s</b>	<b>UEENEEG033A – Solve problems in single and three phase low voltage electrical apparatus and circuits - Heating</b>

2. Calculate the **3 different wattage outputs and combined resistance values** derived from a three heat switch controlling a single-phase 240 volt stove top grill that consists of two 1 kW elements. Please **show** working.

**Low**

\_\_\_\_\_  $\Omega$  \_\_\_\_\_ **W**

**Medium**

\_\_\_\_\_  $\Omega$  \_\_\_\_\_ **W**

**High**

\_\_\_\_\_  $\Omega$  \_\_\_\_\_ **W**



## Portfolio Assessment tool

<b>Qualification national code and title</b>	<b>UEE30811 - Certificate III in Electrotechnology: Electrician</b>
<b>Unit/s national code/s and title/s</b>	<b>UEENEEG033A – Solve problems in single and three phase low voltage electrical apparatus and circuits - Heating</b>

3. Explain how a simmer-stat controller works.

---

---

---

---

---

---

---

4. Draw a circuit diagram of a simmer-stat controlling a hot water urn

5. Is a simmer-stat suitable for use in controlling an oven?

YES NO (Circle correct answer)

Explain your answer.

---

---



**Portfolio Assessment tool**

<b>Qualification national code and title</b>	<b>UEE30811 - Certificate III in Electrotechnology: Electrician</b>
<b>Unit/s national code/s and title/s</b>	<b>UEENEEG033A – Solve problems in single and three phase low voltage electrical apparatus and circuits - Heating</b>

6. Explain the principle of a “vapour (capillary) tube” type thermostat and list one application?

---



---



---



---

Application \_\_\_\_\_

7. What precautions are necessary when handling and installing “vapour” controlled thermostats?

---



---



---

8. Give two applications of where a “fixed temperature” thermostat is an essential component which ensures that the device operates safety and as intended.

---



---

9. State the dangerous situation that may arise if the “Over-temperature” thermostat on a Hot Water System was to be bridged out.

---



---



---



---



**Portfolio Assessment tool**

<b>Qualification national code and title</b>	<b>UEE30811 - Certificate III in Electrotechnology: Electrician</b>
<b>Unit/s national code/s and title/s</b>	<b>UEENEEG033A – Solve problems in single and three phase low voltage electrical apparatus and circuits - Heating</b>

10. If a “Simmer-stat” should become faulty; in which state/s are they most likely to fail?

ON      OFF      HALF ON/ HALF OFF      (Circle the correct answer/s)

There is a special requirement in the “Wiring Rules” to reduce the danger posed by a failed Simmer-stat, what is this requirement?

---



---



---

Provide the AS/NZS3000 clause number \_\_\_\_\_

11. Define ‘HEAT’.

---



---

12. Define ‘TEMPERATURE’.

---



---



## Portfolio Assessment tool

<b>Qualification national code and title</b>	<b>UEE30811 - Certificate III in Electrotechnology: Electrician</b>
<b>Unit/s national code/s and title/s</b>	<b>UEENEEG033A – Solve problems in single and three phase low voltage electrical apparatus and circuits - Heating</b>

13. State the three different types of 'HEAT ENERGY TRANSFER'.

---

---

---

14. Describe three different types of 'HEATING CONTROLLERS'.

---

---

---

15. State two different methods of 'MANUAL HEATING CONTROL'

---

---

16. List three different methods of 'AUTOMATIC HEATING CONTROL' systems.

---

---

---

**END OF ASSESSMENT**