
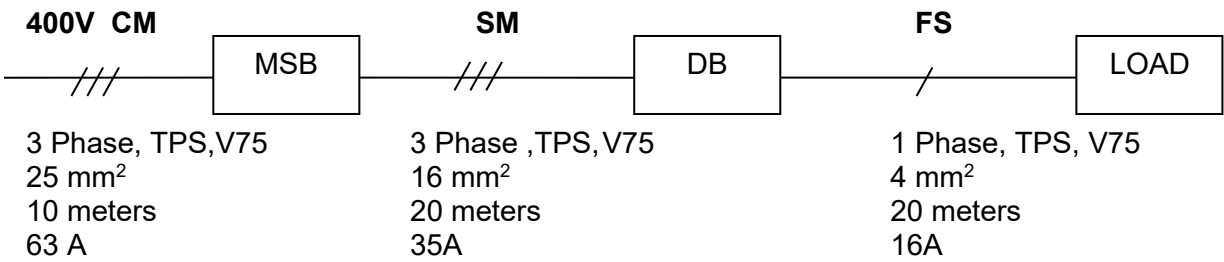


REVISION 3


Question 1 (Find max voltage at load)

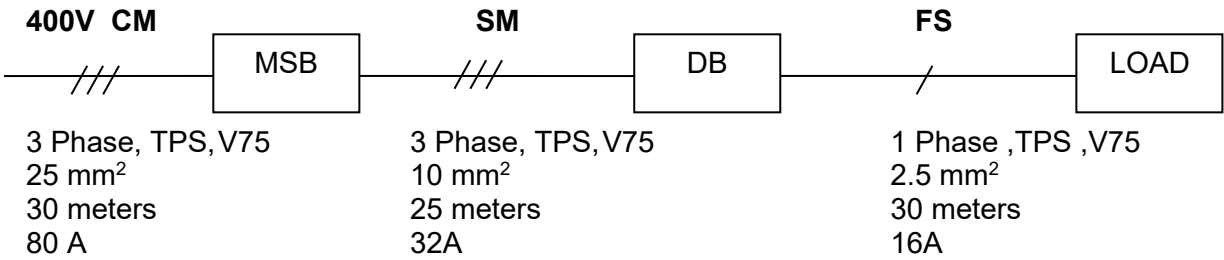


Question 2 (Find max voltage at load)




Question 3 (Find max voltage at load)

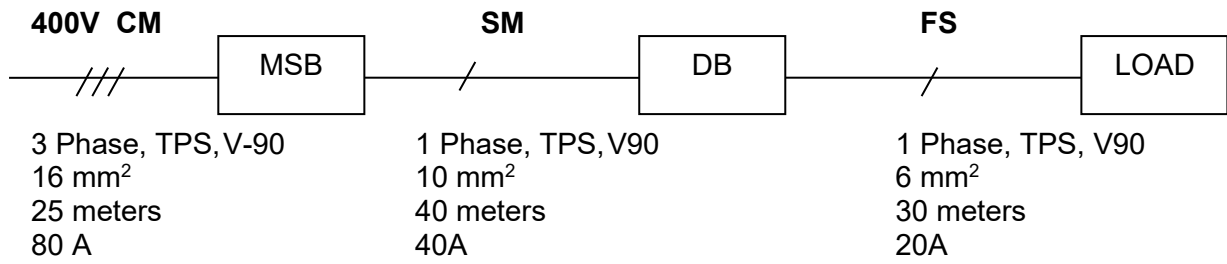

Question 4 (Find max voltage at load)

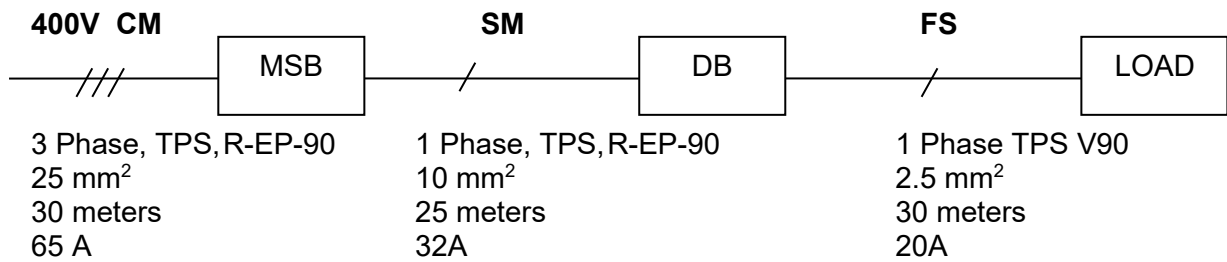

Question 5 (Find max voltage at load)

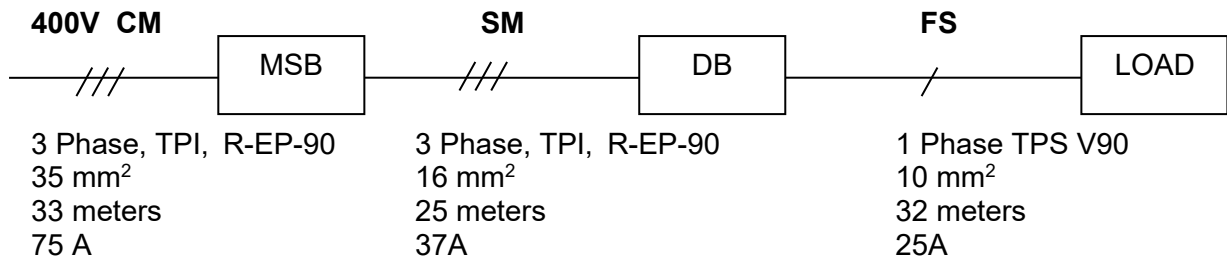

Question 6 (Find max voltage at load)

